

Power in 3-phase system

Prepared by: Ridwan Abrar



Read aloud



Ask Copilot



543

of 1056



We may do this even if the neutral line is absent, as in the three-wire system.

Calculate the line currents in the three-wire Y-Y system of Fig. 12.13.

Example 12.2

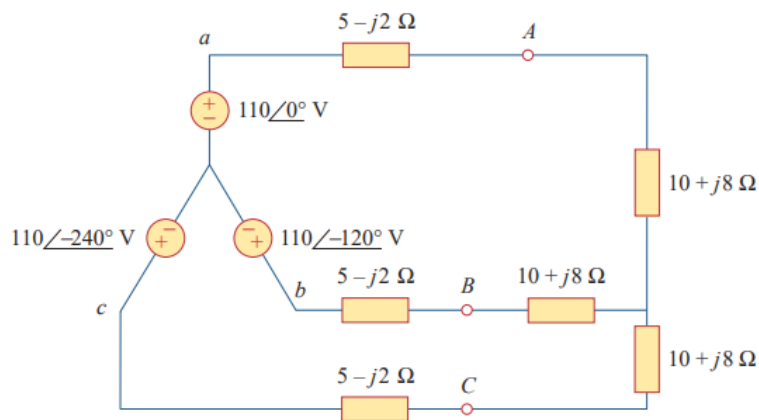


Figure 12.13

Three-wire Y-Y system; for Example 12.2.

Solution:

The three-phase circuit in Fig. 12.13 is balanced; we may replace it with its single-phase equivalent circuit such as in Fig. 12.12. We obtain

Question

- Determine the total power, average power and reactive power at the source and at the load