
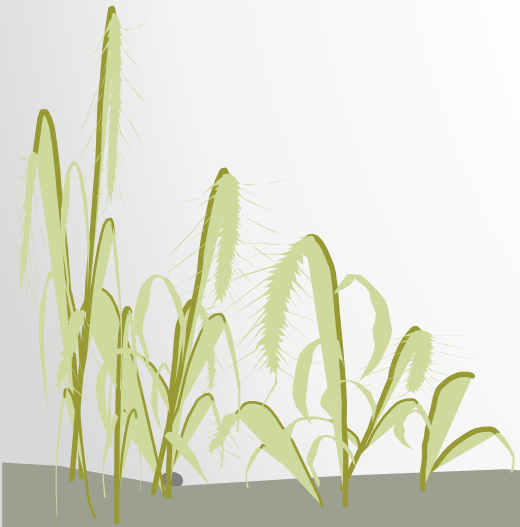


Introduction to Three Phase System

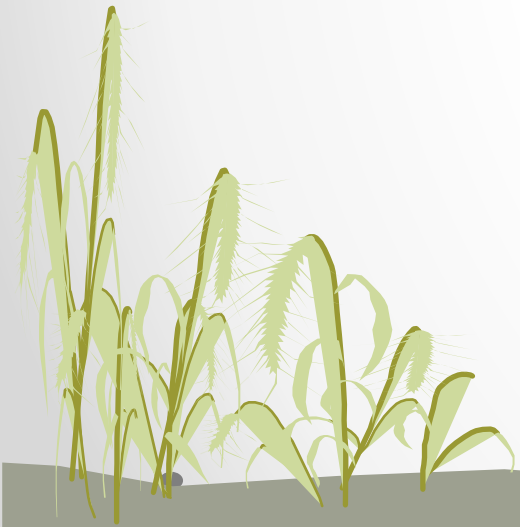


Title and Content Layout with List

- After the ending of this lesson, students are able to know about
 - Wye Delta Configuration with mathematical analysis
 - Delta Delta configuration with mathematical analysis
 - Wattmeter Connection





BALANCED WYE-DELTA CONNECTION

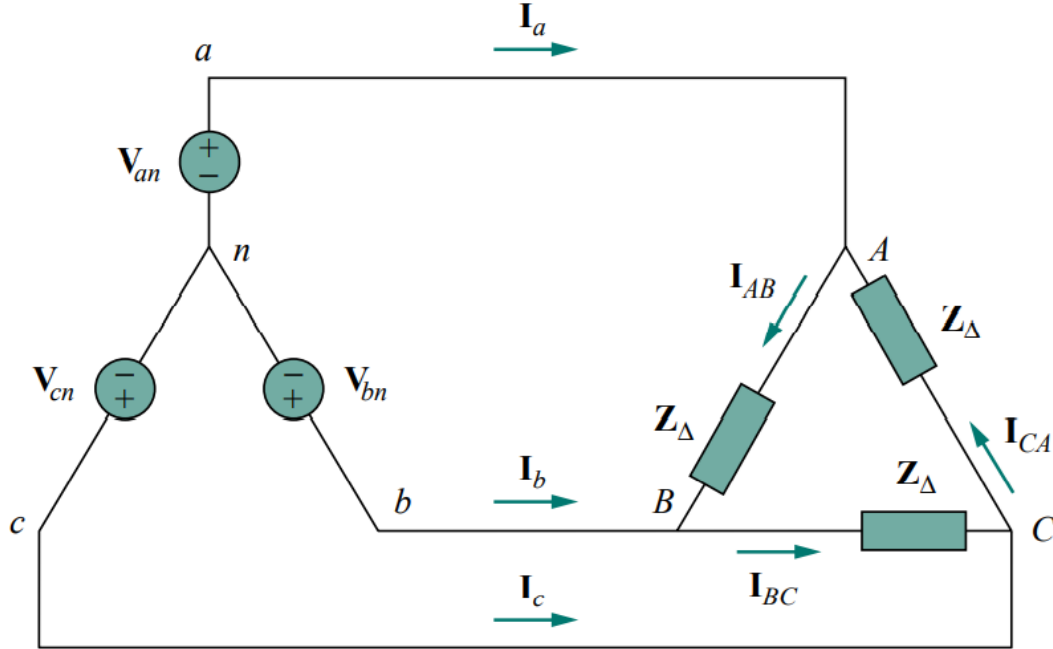

$$V_{an} = V_p \angle 0^\circ$$
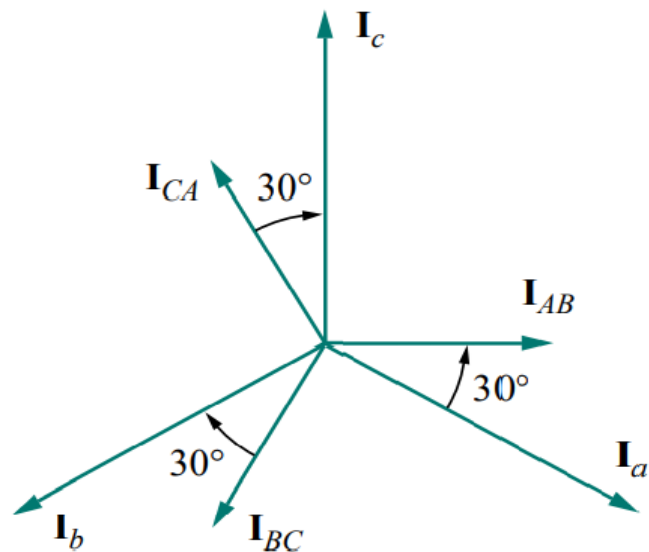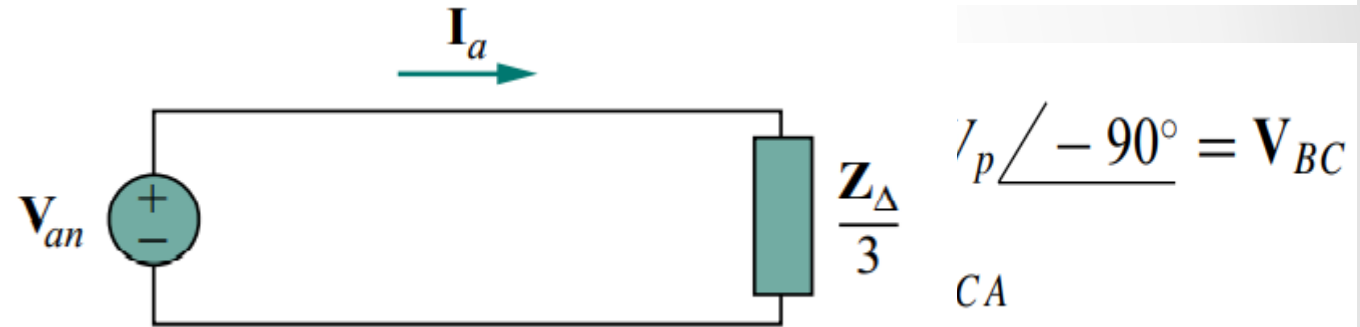
$$V_{bn} = V_p \angle -120^\circ, \quad V_{cn} = V_p \angle +120^\circ$$



$$I_{AB} = \frac{V_{AB}}{Z_{\Delta}}, \quad I_{BC} = \frac{V_{BC}}{Z_{\Delta}}, \quad I_{CA} = \frac{V_{CA}}{Z_{\Delta}}$$

Calculation of line currents

- The line currents are obtained from the phase currents by applying KCL at nodes A, B and C

$$\mathbf{I}_a = \mathbf{I}_{AB} - \mathbf{I}_{CA}, \quad \mathbf{I}_b = \mathbf{I}_{BC} - \mathbf{I}_{AB}, \quad \mathbf{I}_c = \mathbf{I}_{CA} - \mathbf{I}_{BC} \quad (12.23)$$

Since $\mathbf{I}_{CA} = \mathbf{I}_{AB} \angle -240^\circ$,


$$\begin{aligned} \mathbf{I}_a &= \mathbf{I}_{AB} - \mathbf{I}_{CA} = \mathbf{I}_{AB}(1 - 1 \angle -240^\circ) \\ &= \mathbf{I}_{AB}(1 + 0.5 - j0.866) = \mathbf{I}_{AB}\sqrt{3} \angle -30^\circ \end{aligned} \quad (12.24)$$


showing that the magnitude I_L of the line current is $\sqrt{3}$ times the magnitude I_p of the phase current, or

$$I_L = \sqrt{3}I_p \quad (12.25)$$

Problem

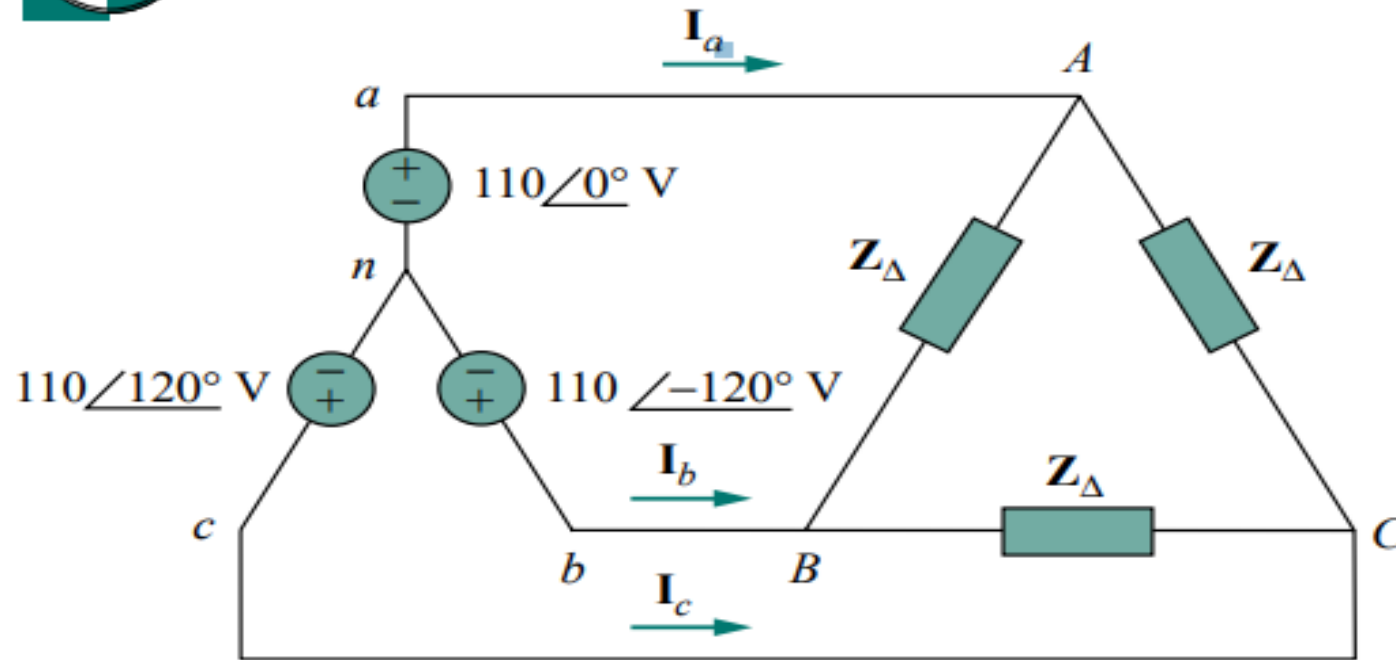12.12 Solve for the line currents in the Y- Δ circuit of Fig. 12.45. Take $Z_{\Delta} = 60 \angle 45^{\circ} \Omega$.



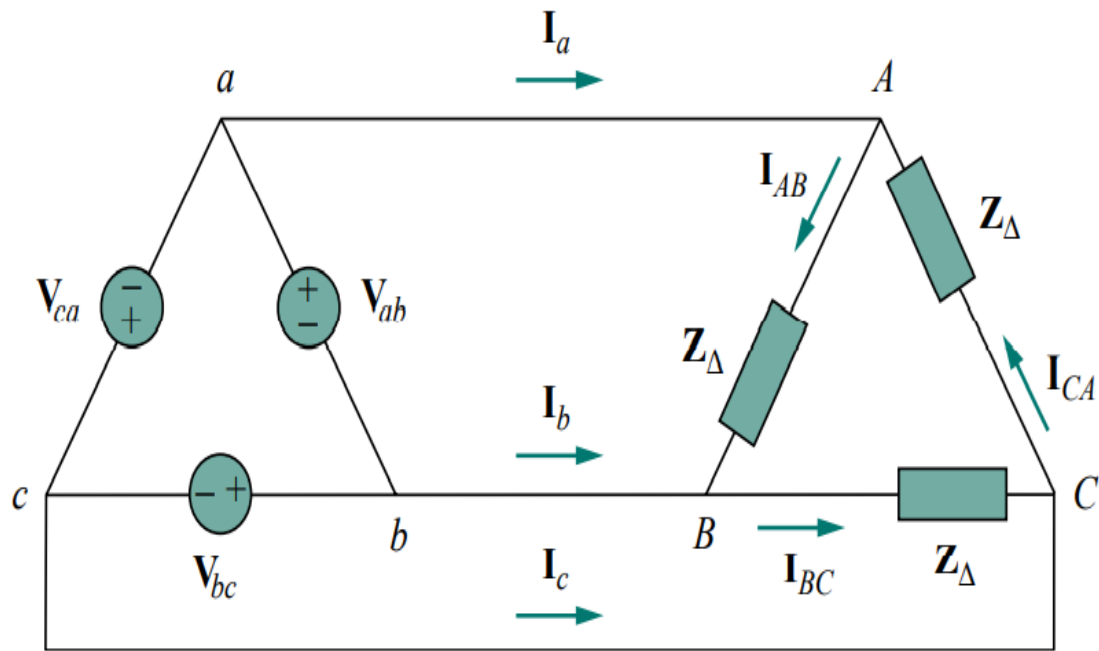

$$V_{ab} = V_{AB}, \quad V_{bc} = V_{BC}, \quad V_{ca} = V_{CA}$$

Hence, the phase currents are


$$I_{AB} = \frac{V_{AB}}{Z_{\Delta}} = \frac{V_{ab}}{Z_{\Delta}}, \quad I_{BC} = \frac{V_{BC}}{Z_{\Delta}} = \frac{V_{bc}}{Z_{\Delta}}$$

$$I_{CA} = \frac{V_{CA}}{Z_{\Delta}} = \frac{V_{ca}}{Z_{\Delta}}$$

How can you calculate I_a , I_b and I_c ?

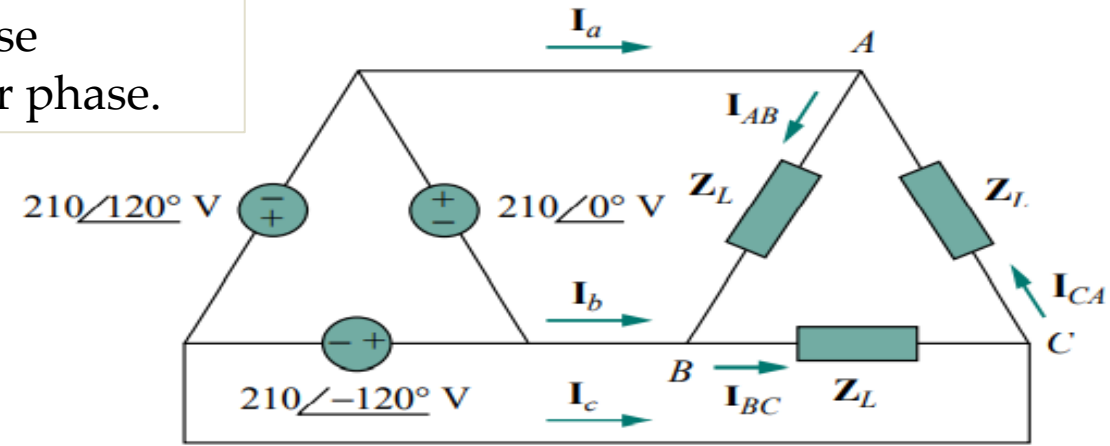Problem

Refer to the circuit in Fig. 12.49. Find the line and phase currents. Assume that the load impedance is $12 + j9$ per phase.



Solution

The load impedance per phase is

$$\mathbf{Z}_{\Delta} = 20 - j15 = 25 \angle -36.87^{\circ} \Omega$$

Since $\mathbf{V}_{AB} = \mathbf{V}_{ab}$, the phase currents are

$$\mathbf{I}_{AB} = \frac{\mathbf{V}_{AB}}{\mathbf{Z}_{\Delta}} = \frac{330 \angle 0^{\circ}}{25 \angle -36.87^{\circ}} = 13.2 \angle 36.87^{\circ} \text{ A}$$

$$\mathbf{I}_{BC} = \mathbf{I}_{AB} \angle -120^{\circ} = 13.2 \angle -83.13^{\circ} \text{ A}$$

$$\mathbf{I}_{CA} = \mathbf{I}_{AB} \angle +120^{\circ} = 13.2 \angle 156.87^{\circ} \text{ A}$$

For a delta load, the line current always lags the corresponding phase current by 30° and has a magnitude $\sqrt{3}$ times that of the phase current.

Hence, the line currents are

$$\begin{aligned} \mathbf{I}_a &= \mathbf{I}_{AB} \sqrt{3} \angle -30^{\circ} = (13.2 \angle 36.87^{\circ})(\sqrt{3} \angle -30^{\circ}) \\ &= 22.86 \angle 6.87^{\circ} \text{ A} \end{aligned}$$

$$\mathbf{I}_b = \mathbf{I}_a \angle -120^{\circ} = 22.86 \angle -113.13^{\circ} \text{ A}$$

$$\mathbf{I}_c = \mathbf{I}_a \angle +120^{\circ} = 22.86 \angle 126.87^{\circ} \text{ A}$$

Balanced Delta-Wye Connection

- A balanced Delta-Wye system consists of a balanced Delta-connected source feeding a balanced Wye-connected load
- Phase voltages, as well as line voltages

$$\begin{aligned}V_{ab} &= V_p \angle 0^\circ, & V_{bc} &= V_p \angle -120^\circ \\V_{ca} &= V_p \angle +120^\circ\end{aligned}$$

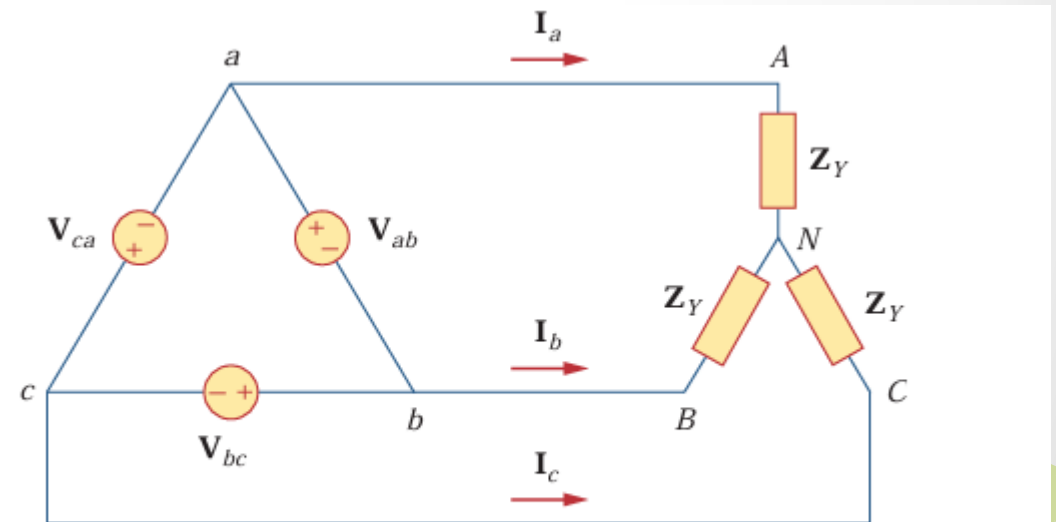


Figure 12.18

A balanced Δ -Y connection.

Line currents

We can obtain the line currents in many ways. One way is to apply KVL to loop $aANBba$ in Fig. 12.18, writing

$$-V_{ab} + Z_Y I_a - Z_Y I_b = 0$$

or

$$Z_Y(I_a - I_b) = V_{ab} = V_p \angle 0^\circ$$

Thus,


$$I_a - I_b = \frac{V_p \angle 0^\circ}{Z_Y}$$

But I_b lags I_a by 120° , since we assumed the abc sequence; that is, $I_b = I_a \angle -120^\circ$. Hence,

$$\begin{aligned} I_a - I_b &= I_a(1 - 1 \angle -120^\circ) \\ &= I_a \left(1 + \frac{1}{2} + j \frac{\sqrt{3}}{2} \right) = I_a \sqrt{3} \angle 30^\circ \end{aligned} \quad (12.36)$$

Substituting Eq. (12.36) into Eq. (12.35) gives
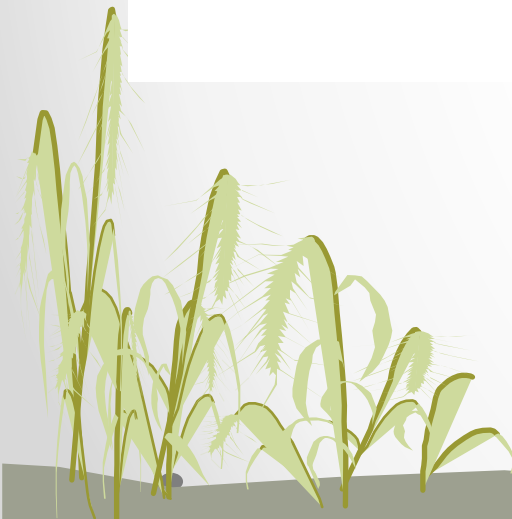
$$I_a = \frac{V_p / \sqrt{3} \angle -30^\circ}{Z_Y} \quad (12.37)$$



Problem (Delta-Wye System)


- A balanced Y-connected load with a phase impedance of $40+j25$ Ohms is supplied by a balanced, positive sequence Delta-connected source with a line voltage of 210 V. Calculate the phase currents. Use V_{ab} as reference.

Answer:

$$I_a = 2.57 \angle -62^\circ$$

$$I_b = 2.57 \angle -178^\circ$$

$$I_c = 2.57 \angle 58^\circ$$

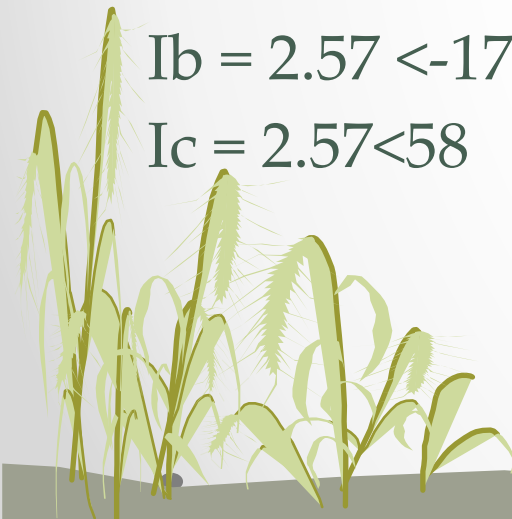

Book solution

Solution:

The load impedance is

$$\mathbf{Z}_Y = 40 + j25 = 47.17 \angle 32^\circ \Omega$$

and the source voltage is

$$\mathbf{V}_{ab} = 210 \angle 0^\circ \text{ V}$$

When the Δ -connected source is transformed to a Y-connected source,

$$\mathbf{V}_{an} = \frac{\mathbf{V}_{ab}}{\sqrt{3}} \angle -30^\circ = 121.2 \angle -30^\circ \text{ V}$$


The line currents are

$$\mathbf{I}_a = \frac{\mathbf{V}_{an}}{\mathbf{Z}_Y} = \frac{121.2 \angle -30^\circ}{47.12 \angle 32^\circ} = 2.57 \angle -62^\circ \text{ A}$$

$$\mathbf{I}_b = \mathbf{I}_a \angle -120^\circ = 2.57 \angle -178^\circ \text{ A}$$

$$\mathbf{I}_c = \mathbf{I}_a \angle 120^\circ = 2.57 \angle 58^\circ \text{ A}$$

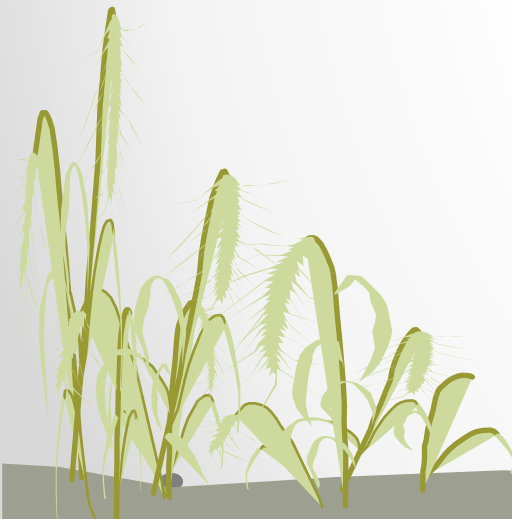which are the same as the phase currents.




- Please carry a printed copy of this page while working on problems related to three-phase systems
- Memorise this part, **very very important**

Summary of phase and line voltages/currents for balanced three-phase systems.¹

Connection	Phase voltages/currents	Line voltages/currents
Y-Y	$V_{an} = V_p/0^\circ$ $V_{bn} = V_p/-120^\circ$ $V_{cn} = V_p/+120^\circ$ Same as line currents	$V_{ab} = \sqrt{3}V_p/30^\circ$ $V_{bc} = V_{ab}/-120^\circ$ $V_{ca} = V_{ab}/+120^\circ$ $I_a = V_{an}/Z_Y$ $I_b = I_a/-120^\circ$ $I_c = I_a/+120^\circ$
Y-Δ	$V_{an} = V_p/0^\circ$ $V_{bn} = V_p/-120^\circ$ $V_{cn} = V_p/+120^\circ$ $I_{AB} = V_{AB}/Z_\Delta$ $I_{BC} = V_{BC}/Z_\Delta$ $I_{CA} = V_{CA}/Z_\Delta$	$V_{ab} = V_{AB} = \sqrt{3}V_p/30^\circ$ $V_{bc} = V_{BC} = V_{ab}/-120^\circ$ $V_{ca} = V_{CA} = V_{ab}/+120^\circ$ $I_a = I_{AB}\sqrt{3}/-30^\circ$ $I_b = I_a/-120^\circ$ $I_c = I_a/+120^\circ$
Δ-Δ	$V_{ab} = V_p/0^\circ$ $V_{bc} = V_p/-120^\circ$ $V_{ca} = V_p/+120^\circ$ $I_{AB} = V_{ab}/Z_\Delta$ $I_{BC} = V_{bc}/Z_\Delta$ $I_{CA} = V_{ca}/Z_\Delta$	Same as phase voltages $I_a = I_{AB}\sqrt{3}/-30^\circ$ $I_b = I_a/-120^\circ$ $I_c = I_a/+120^\circ$
Δ-Y	$V_{ab} = V_p/0^\circ$ $V_{bc} = V_p/-120^\circ$ $V_{ca} = V_p/+120^\circ$ Same as line currents	Same as phase voltages $I_a = \frac{V_p/-30^\circ}{\sqrt{3}Z_Y}$ $I_b = I_a/-120^\circ$ $I_c = I_a/+120^\circ$

Wattmeter Related Math

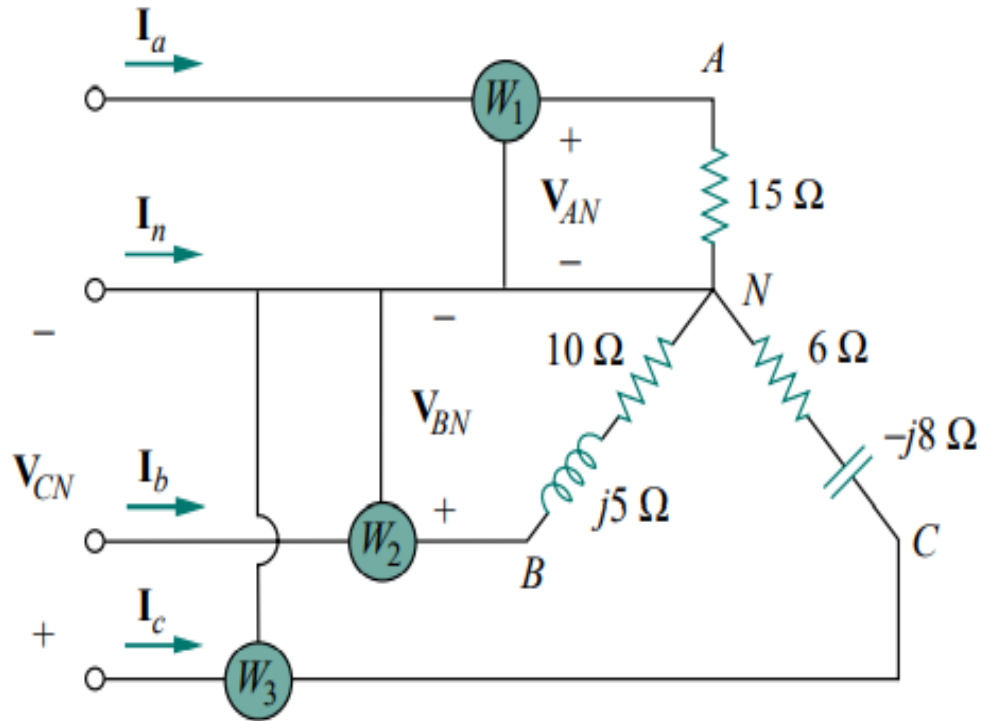

$$V_{AN} = 100 \angle 0^\circ, \quad V_{BN} = 100 \angle 120^\circ, \quad V_{CN} = 100 \angle -120^\circ \text{ V}$$

while

$$I_a = 6.67 \angle 0^\circ, \quad I_b = 8.94 \angle 93.44^\circ, \quad I_c = 10 \angle -66.87^\circ \text{ A}$$

Predict the wattmeter readings.

